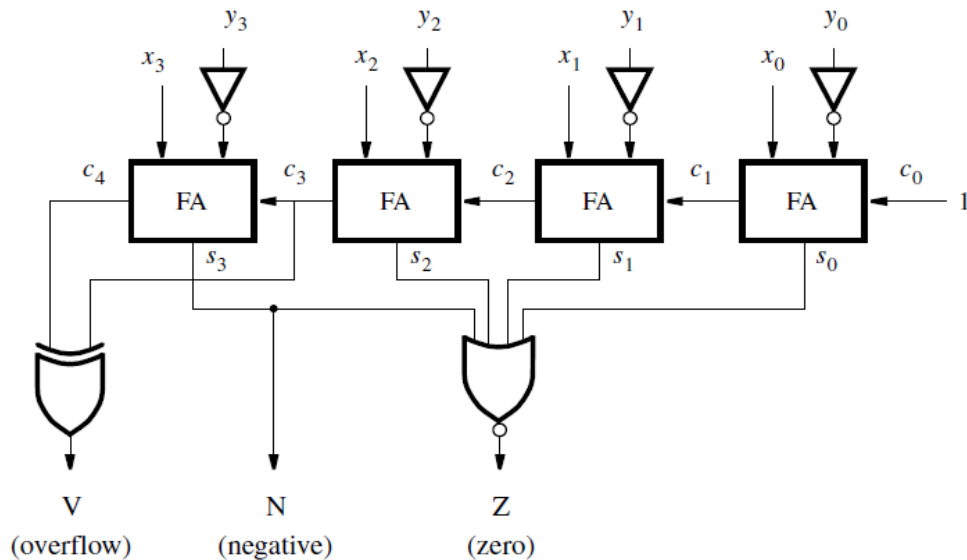


### Verilog Lab Level 1.2

- Q1. 8x1 Multiplexer using 2\*1 Multiplexer  
Q2. 1x8 demultiplexer using 1\*2 Demultiplexer.  
Q3. 4x16 Decoder using 2x4.  
Q4. 16x4 Encoder using 4x2.  
Q5. n-to-2<sup>n</sup> decoder (Hint: using for loop)  
Q6. Design a 8-to-3 Priority Encoder:  
(a) using Casex  
(b) using for loop  
Q7. 4 - bit Ripple Carry Adder  
Q8. N-bit Ripple Carry Adder (Generic ripple Carry Adder)  
(a) using for loop  
(b) using instantiation of 1-bit full adder (Hint: use generate construct)  
(c) using arithmetic assignment statement  
Q9. Adder- Subtractor circuit  
Q10. Design a one-digit BCD adder.  
Q11. Design following Code converters using verilog:  
(a) Binary to Gray Converter  
(b) Gray to Binary Converter  
(c) BCD to seven segment converter  
Q12. Parity Generator and Parity Checker  
Q13. design a 4-bit comparator using relational operators.  
Q14. Write verilog code to specify the 4-bit comparator circuit shown in following figure:




- Q15. Design an 4-bit ALU which performs the following functions:

- (a) Add      (b) Subtract      (c) XOR      (D) OR      (E) Invert      (F)AND  
 (G) Multiplication      (h) Division

Q16. Design a 16\*1 multiplexer using 4\*1 with the following styles:

- (a) using module instantiation  
 (b) using tasks  
 (c) using functions

 Q17. Write verilog code that represents the following circuit. [Hint: use 2\*4 decoder module as a subcircuit in your code]



Q18. Write Verilog code that represents the following shifter circuit:

