 


Verilog Lab Level 1.1


Design the following combinational circuits.

Q1. Write Verilog code for given circuits.

(a)



(b)

 

Q2. (a) Write Verilog code for given Equation $F = x_1x_3' + x_2x_3' + x_3'x_4' + x_1x_2 + x_1x_4'$

(b) Write Verilog code for given Equation $F = (x_1+x_3').(x_1+x_2+x_4').(x_2+x_3'+x_4')$

(c) Write verilog code to implement the function $f(x_1, x_2, x_3, x_4) = \sum m(0,1,2,4,5,7,8,9,11,12,14,15)$. Ensure that the resulting circuit is as simple as possible.

(d) Write verilog code to implement the function $f(x_1, x_2, x_3, x_4) = \sum m(1,4,7,14,15) + D(0,5,9)$. Ensure that the resulting circuit is as simple as possible.

(e) Write verilog code to implement the function $f(x_1, x_2, x_3, x_4) = \pi M(6,8,9,12,13)$. Ensure that the resulting circuit is as simple as possible.

(f) Write verilog code to implement the function $f(x_1, x_2, x_3, x_4) = \pi M(3, 11, 14) + D(0,2,10,12)$. Ensure that the resulting circuit is as simple as possible.

- Q3. 4x1 Multiplexer
Q4. 1x4 Demultiplexer.
Q5. 3x8 Decoder.
Q6. 8x3 Encoder.
Q7. Design a 4*1 Multiplexer using conditional operator.
Q8. Half Adder.
Q9. Full Adder.
Q10. Half Subtractor.
Q11. Full Subtractor

Q12. Consider the following program:

```
module adder sign (X, Y, S, S2s);  
    input [3:0] X, Y;  
    output [7:0] S, S2s;  
    assign S = X + Y,  
          S2s = {{4{X[3]}}, X} + {{4{Y[3]}}, Y};  
endmodule
```

- (a) if X = 0011 and Y = 1101, What will be the value of S and S2s?
(b) What operation is assigned for S2s in the given program.